
2025/10/22 15:36 1/6 ain\_4\_board\_parts\_list

# AIN\_4 module

This is a simple way of scaling CVs (as might come from a modular) ready for an STM322F4 Core module.

## **Schematic**

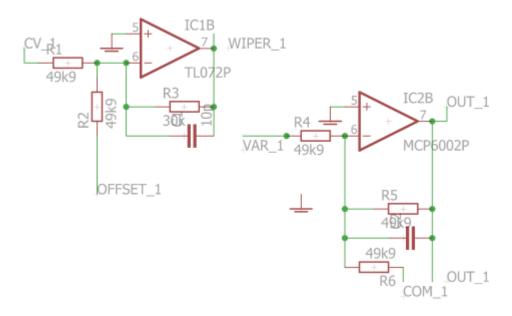

The circuit is a very simple series of two inverting amplifiers per channel. The first is a TL072 powered from +12/-12V, while the second is an MCP6002 powered from 3v3/0V (ground). It's possible to preset the ranges (see below) but it's probably more useful to use the associated Control Board.

### **BOM**

Туре	Qty	Value	Package	Parts	Notes
resistors					
	20	49k9	0204/7	R1, R2, R4, R5, R6, R7, R8, R10, R11, R12, R13, R14, R16, R17, R18, R19, R20, R22, R23, R24	
	4	30k	0204/7	R3, R9, R15, R21	nominal gain can be adjusted e.g. (22k/49.9k)*5V = 2.2V
capacitors					
	4	10p	025×050	C1, C3, C5, C7	
	9	100n	025×050	C10, C12, C13, C14, C15, C16, C17, C18, C20	remove 1 if powering from Core
	3	10u	electrolytic 2,5-6	C9, C11, C19	remove 1 if powering from Core

Туре	Qty	Value	Package	Parts	Notes
resistors					
	4	optional	025×050	C2, C4, C6, C8	can use another e.g. 10pF cap here for more filtering
inductors					
	2	BEAD	5MM	L1, L2	
ICs					
	2	MCP6002P	DIL08	IC2, IC4	sockets are recommended
	2	TL072P	DIL08	IC1, IC3	sockets are recommended
Vreg					
	1	optional	TO-220	VR1	remove if powering from Core
headers					
	7		1X02_SMALL	JP1, JP2, JP3, JP4, JP5, JP6, JP7	check board for headers as SIL strips of 3, 5 or 6
	8		1X03_SMALL	JP8, JP9, JP10, JP11, JP12, JP13, JP14, JP15	
	2		2*5 (shrouded)	J1, J2	

# **Assembly**


Putting the board together is simple. As usual, start with the flattest components and work your way up.

#### **Resistors**

Four 30k resistors as marked, the remainder are 49k9. For best results, match R1/R2, R7/R8 (and so on), and R4/R5/R6, R10/R11/R12 (and so on). The value is less important than the minimum deviation.


http://wiki.midibox.org/ Printed on 2025/10/22 15:36

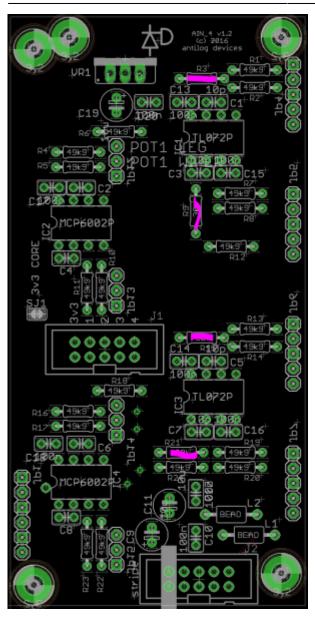2025/10/22 15:36 3/6 ain\_4\_board\_parts\_list


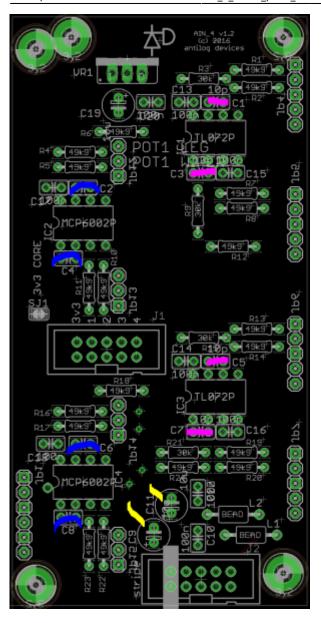
# Capacitors

Four 10p as marked in pink, electrolytics in yellow, blue are optional. Remainder are 10n.




### **Power**

Standard Eurorack header. Red = -12V, Blue = +12V, Green = 0V(ground). For Core power, bridge the yellow solder jumper, otherwise install the Vreg circuit in pink

http://wiki.midibox.org/ Printed on 2025/10/22 15:36

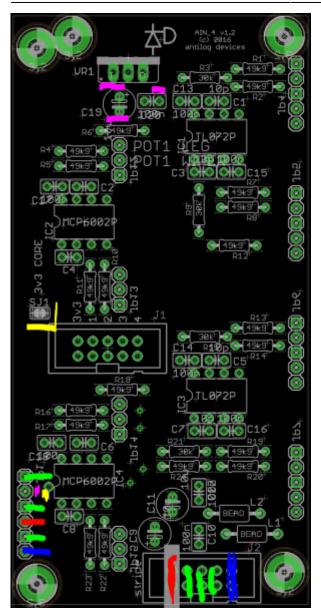2025/10/22 15:36 5/6 ain\_4\_board\_parts\_list



#### Standalone use

For simplest results, use the complementary Control Board. Otherwise see below for header functions.  $===Five\ pin\ header===For\ scaling\ bipolar\ CVs,\ connect\ or\ switch\ into\ OFFSET\ (e.g.\ +5V)$  For 0-5V operation, leave SWITCH open; for 0-10V operation, jumper or switch in SWITCH



 $\blacksquare ===$  Three pin header === With a 100k pot facing you,

solder the left leg to 0V(ground) the centre to WIPER and the right to LEG. WIPER and LEG may be jumpered if pots aren't desired, but it is quite useful to have an attenuator to trim down variable CVs

or even clip the second op amp for crunchy waveforms!  $\blacksquare$  Interconnection to Core ==== J1 carries the scaled CV to J5A or J5B of an STM32F4 Core module. —- ==== License ==== Currently the design is © 2016 antilog devices with all rights reserved; all documentation is CC BY-NC-SA 3.0.

From:

http://wiki.midibox.org/ - MIDIbox

Permanent link:

http://wiki.midibox.org/doku.php?id=ain\_4\_board\_parts\_list&rev=1470844390





http://wiki.midibox.org/ Printed on 2025/10/22 15:36