2025/11/05 07:16 1/3 SEQv4+ Jog module


SEQv4+ Jog module

A BLM using 18 illuminated MEC switches placed around an encoder (datawheel). Two spare DIN pins can accommodate a footswitch and a modular gate.

Schematic

The circuit is a BLM, but only four DIN columns are used. The other four DIN pins scan an encoder and two inputs intended as footswitch/gate. Standard SRIO in on J89 and chained out on J89A.

The BLM is as follows:

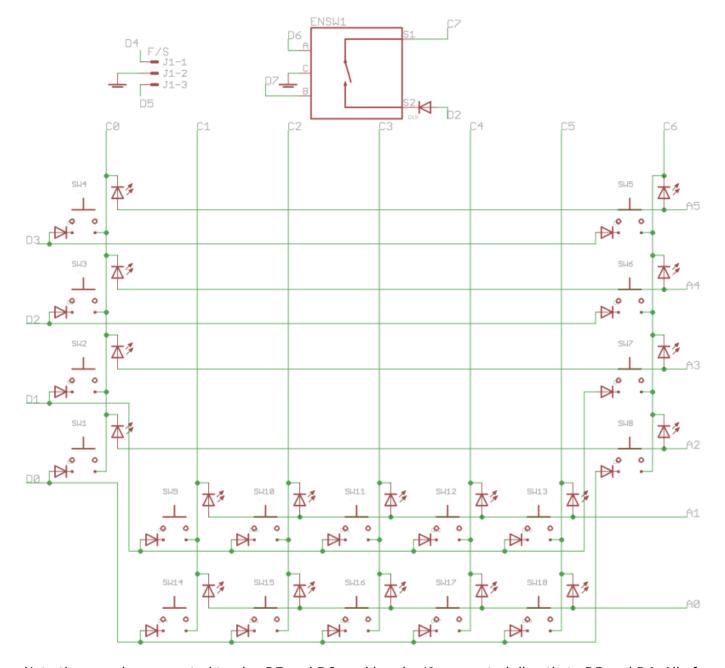

Note the encoder connected to pins D7 and D6, and header J1 connected directly to D5 and D4. All of the cathode rows are used, even C7 just for the encoder push switch.

Only six DOUT anode columns are used. These are current limited by resistors R1-6.

BOM v1.0

Туре	Qty	Value	Package	Parts	Mouser	Reichelt	Conrad	Other	Notes
Resis	tors	•			•				
	6	100-220R 5%	тнт	R1-6					
Resis	tor i	network		-				-	_
	1	10k	SOM16	RN1	4816P-T02-103LF				
Capa	cito	'S							
	3	100n	1206	C1-3					
Diod	es								
	19	1N4148	THT						
LEDs									
	18	various	3mm						insert into switches
ICs									
	1	74HC165	SOIC16	IC2	595-SN74HC165DR				
	2	74HC595	SOIC16	IC1, IC3					
Enco	der								
	1	STEC12				STEC12E08			
Swite	ches								
	18	MEC/APEM	3FTH9	SW1-18	642-3FTH9	TASTER 3FTH9	705276 - 62		
Head	lers	-		-			-	-	_
	1	1*3	male						
	2	2*5	male						
Hard	ware	•							
	6	M3 spacer	TBD						
	1	datawheel	DK-38?						
	18	switchcaps	22.5mm		642-1S11-22.5		1S11-22.5		

Versions

v1.0: first release.

Assembly

Start with the SMT parts (caps, ICs and RN), then the resistors and diodes with correct polarity. Headers, switches (read below first!), encoder, caps and knobs.


Important: insert the LEDs into the switches before soldering them! It's quite hard to bend the legs once the switches are in place. The LED legs should not interfere with the switch action; i.e. the

http://wiki.midibox.org/ Printed on 2025/11/05 07:16

2025/11/05 07:16 3/3 SEQv4+ Jog module

button should be pressed and released without getting caught on the legs.

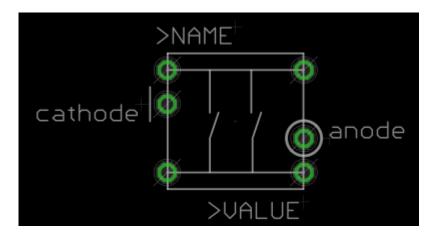Ensure that when the switch is soldered in, the LED is correctly polarised. Round part (anode) of the LED to the circled pin; flat part (cathode) to the line:



License

Currently the design is $\ \odot$ 2017 antilog devices with all rights reserved; all documentation is CC BY-NC-SA 3.0.

From:

http://wiki.midibox.org/ - MIDIbox

Permanent link:

http://wiki.midibox.org/doku.php?id=seqv4plus_jog&rev=1505244245

Last update: 2017/09/12 19:24

