

XYZ-IR-Controller

Hack a Alesis PhotonX25 XYZ-Dome-IR controller
or how to DIY




Introduction

The XYZ Dome works with 1 IR DIODE, and 4 IR Transistors, which are connected to 2x Stereo Audio ADC 24Bit running on Wordclock...


I dont know if i can get the Alesis ADCs running (AL1101) - see Datasheet [al1101-datasheet.pdf](#)
maybe i only remove the DACs and connect them to J5A!

PCB/Schematic

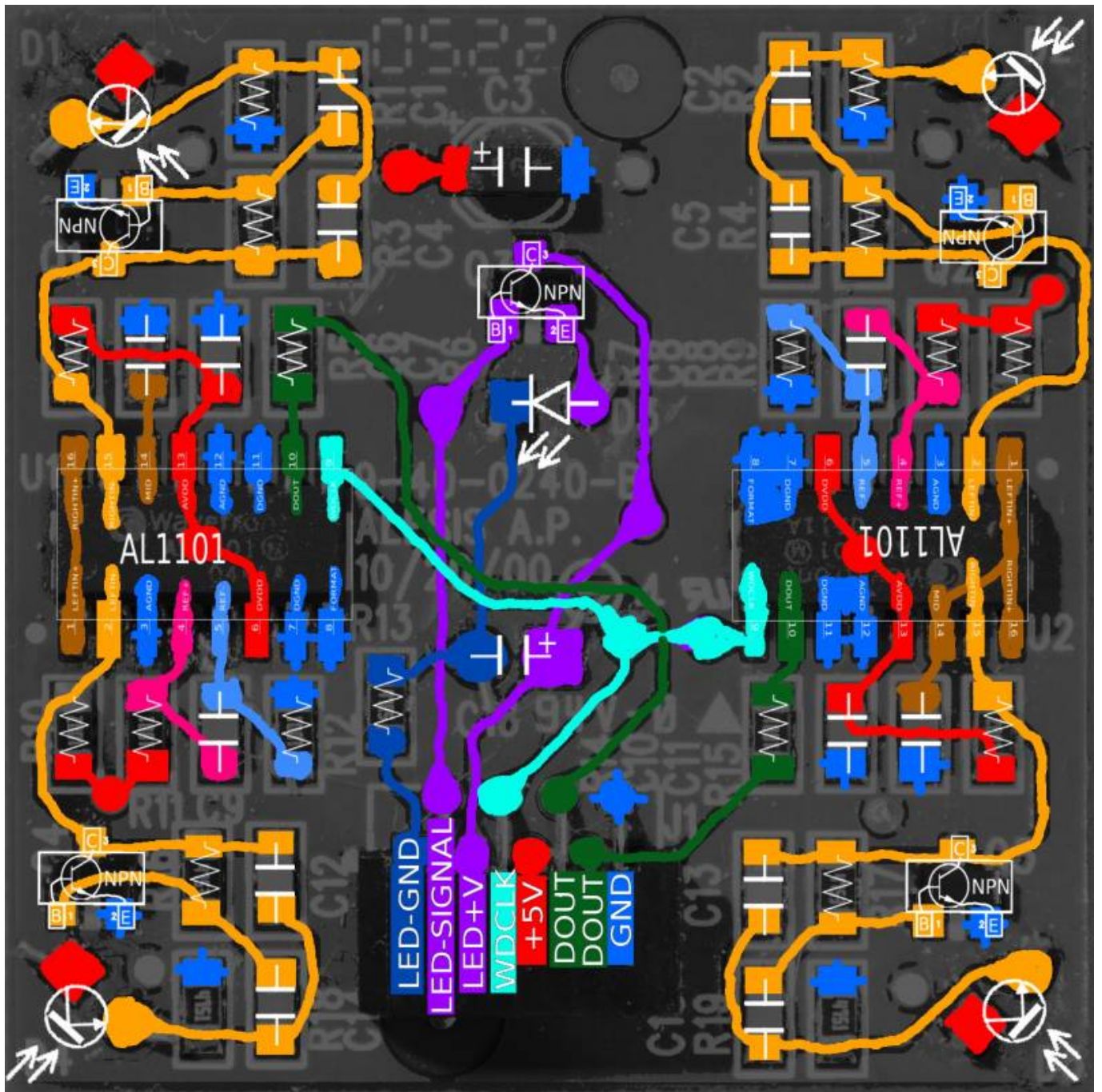first a took a shot of the Front&Back of the IR-PCB... then i matched it, and redrewed every path...




i removed the original picture:

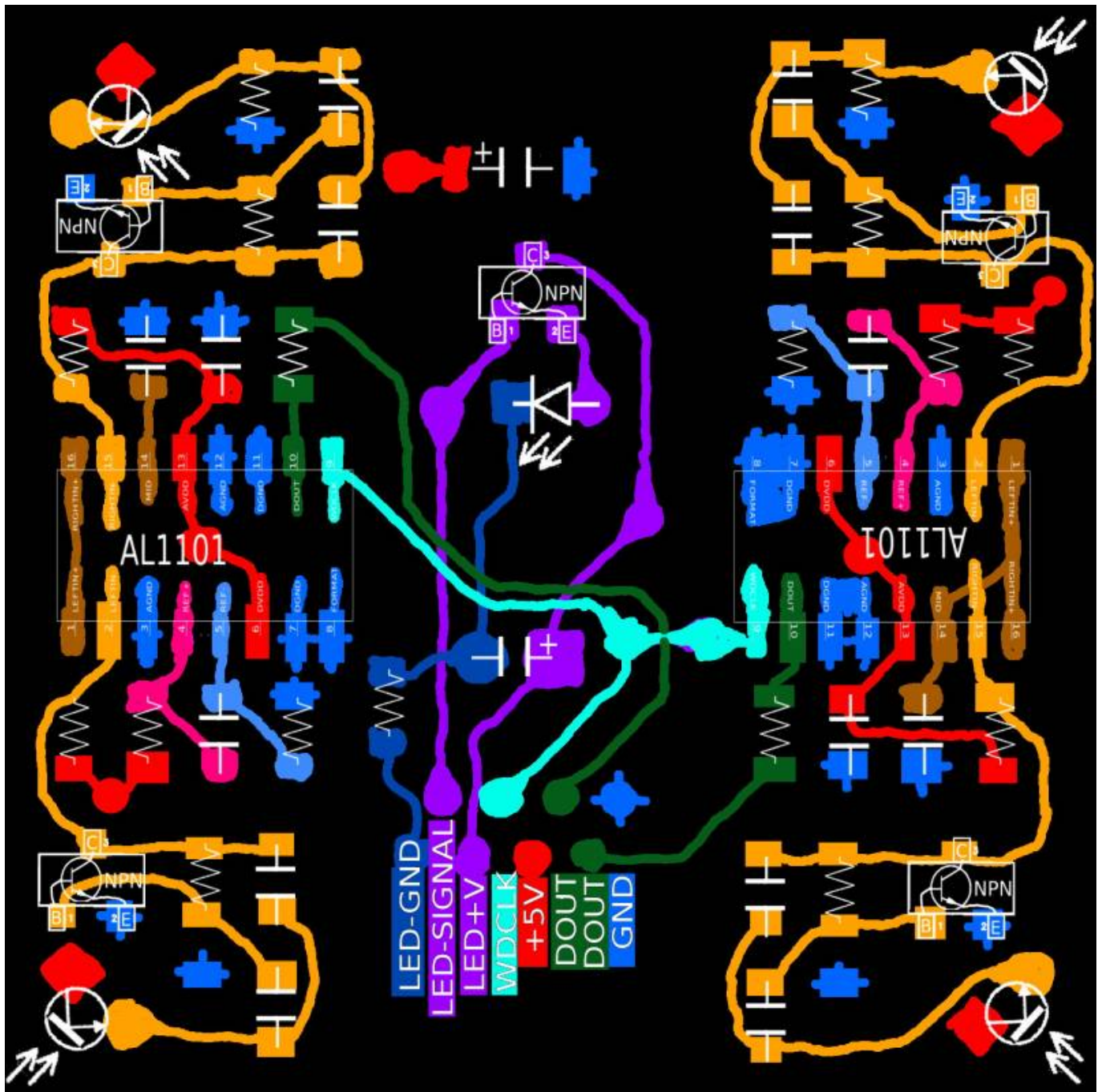

MB MODs

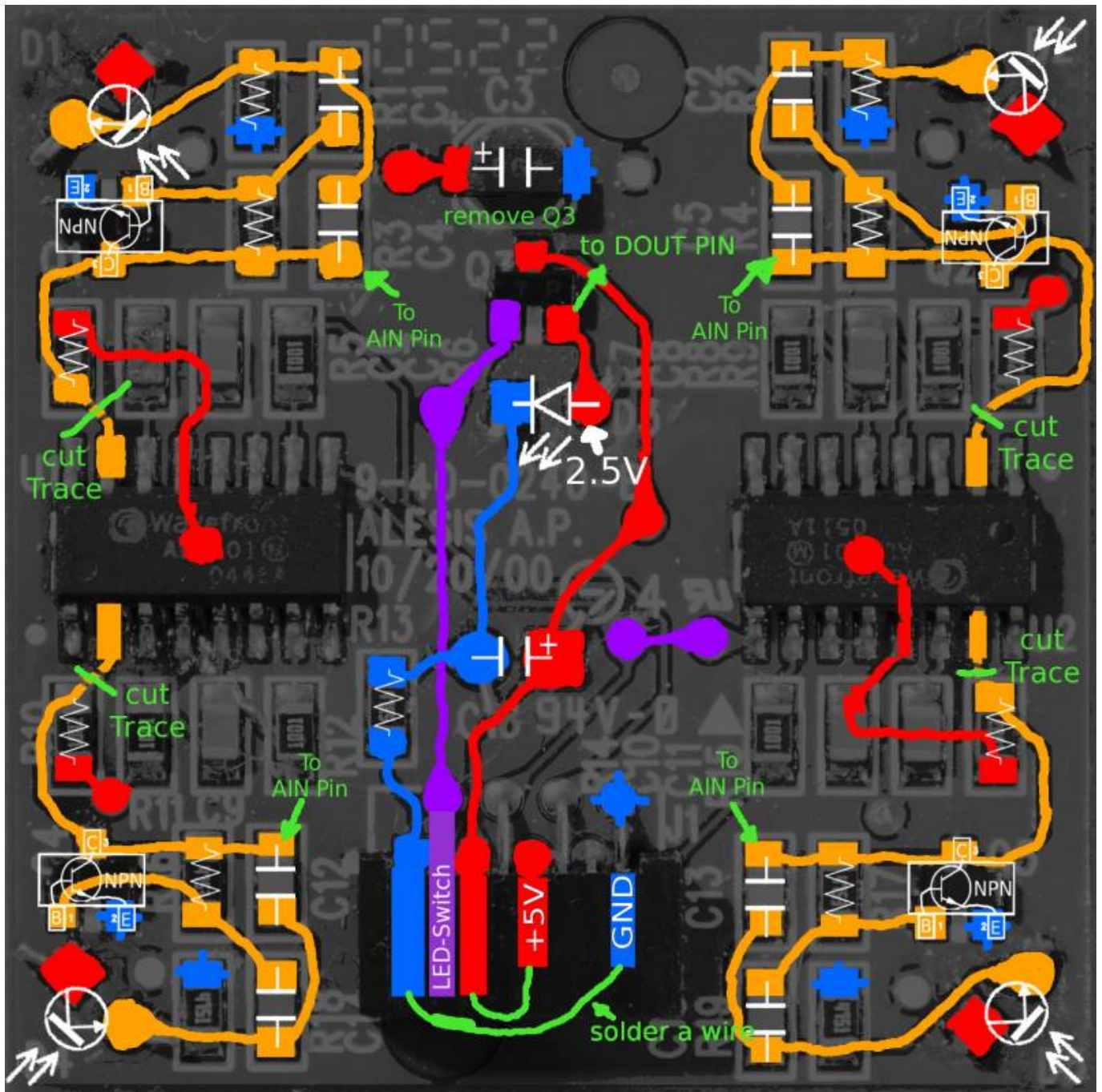How to get it working without touching a SERIAL PROTOCOL?
dont using the onboard DACS, instead use the MB-Core STM32F4 J5A AIN-Port....



Negative: using a lot of bandwidth.

I connected all 4 IR-Transistor-Circuit directly to J5A
The IR-Diode I connected to Pin1 of J10A.

Hardware Requirements

Midibox:

- [core32](#)
- [1xMidi IO](#) connect 1 midicontroller and 1 Note/Clock-Source/Destination

To Do

all...!

Community users working on it

- **Phatline** = Programming, Documentation...

From:

<http://wiki.midibox.org/> - **MIDIbox**

Permanent link:

<http://wiki.midibox.org/doku.php?id=xyz-ir-controller>

Last update: **2020/02/09 05:14**

