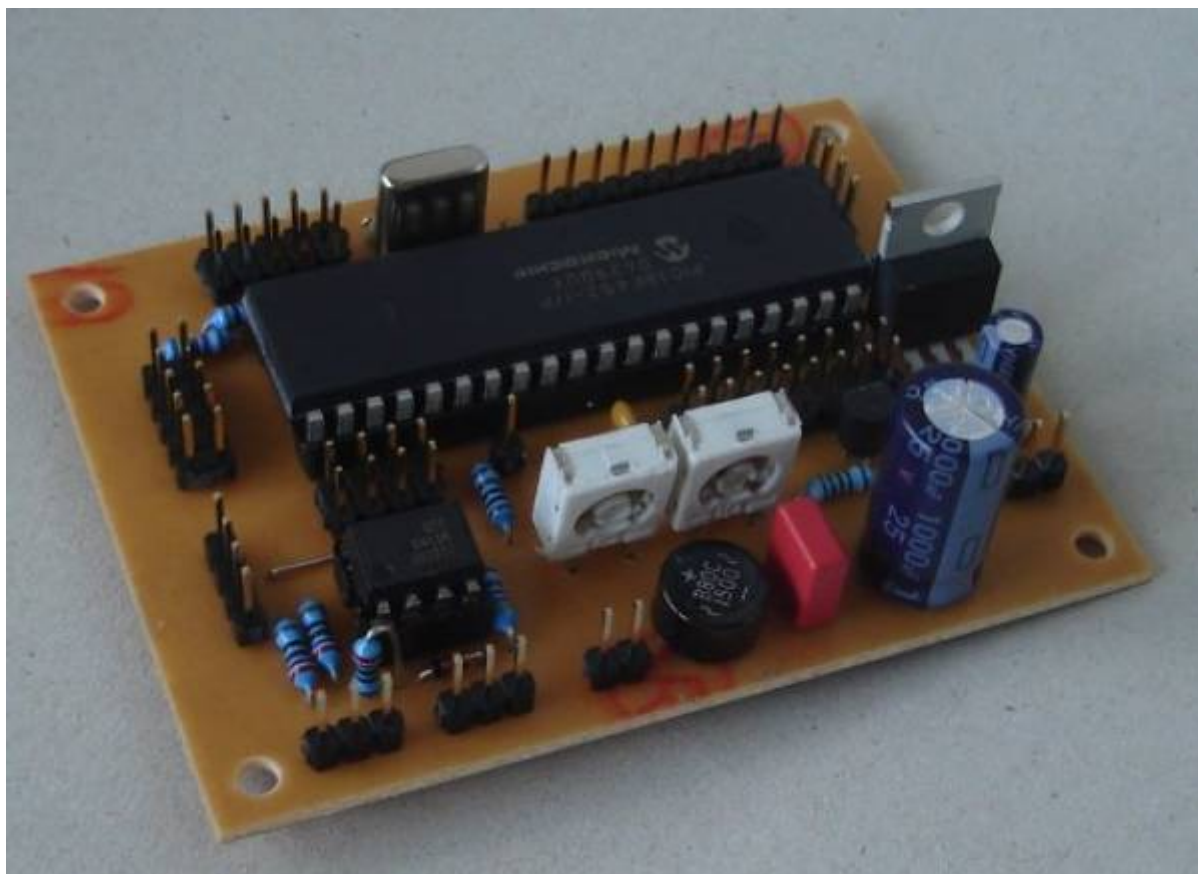


# MBHP Core8 Module

## Introduction

The **MBHP Core Module** is the heart and brain of every **MIDIbox**. It holds the *PIC* microcontroller which runs **MIOS** and your MIDIbox application. It handles **MIDI communication, it drives an LCD (or two), and it connects to all the other modules.**

The PIC is a “**system on chip**” (**SoC**), this means, it contains not only a CPU, but also an **integrated 32k flash program memory, 1536 bytes data memory, 256 bytes data EEPROM, and a lot of usefull peripherals like AD-converter and UART (for MIDI)**. The low prices and worldwide availability for hobbyists makes it a good choice.



Main part of this module is the PIC, a microcontroller manufactured by Microchip. It is clocked at 40 MHz (externally with a 10 MHz crystal) and offers enough performance to handle analog and digital modules with latencies below 1ms.

In distance to other (more modern) microcontrollers, the **PIC is easy to program, requires no external memories, is almost non-destroyable and comes in a handy DIP package**, so that also electronic beginners can work with this chip without the danger of damaging small SMD pins within some seconds with their soldering iron.

If you are planning to program your own application, it's recommended to use a PIC18F452 for highest

compatibility with existing MIDiboxes, a **PIC18F4620 for RAM intensive projects** (64k flash, 1k EEPROM, 3968 bytes RAM), or a **PIC18F4685 for code intensive projects** (96k flash, 1k EEPROM, but only 3328 bytes RAM - provides CAN interface

## Parts

- [Core Board Parts List](#)

## Inputs/Outputs Table

Port	Pins #	Description
J1	2	Connection to PSU. 7V-10VAC transformer, or a wall adapter. At least 500 mA is recommended, AC or DC doesn't matter, since the rectifier behind J1 converts to DC anyhow. Also the polarity has not to be taken into account.
J2	2	

**+5V input:** for supplying from J2 of another core module, or from an external stabilized Power Supply Unit (PSU). In both cases the voltage regulator (IC3) should not be connected, also the rest of the voltage stabilization circuit between J1 and J2 (X1, C5, C6) can be left out. If the core module (and all connected modules to this branch) drains more than 100 mA, it's recommended to mount C5 directly to J2 (a small cable between the outer soldering pads of the left-out 7805 will do this).|

## PIC Microcontrollers

The Core Module can be equipped with following microcontrollers:

- [PIC18F4620](#) *required for MIDibox SEQ V3, possible future default*
- [PIC18F4685](#) *required for MIDibox SID V2 due to the CAN peripheral*

## Multiple Cores

There are different possibilities to have multiple Cores.

- [MIDibox Link](#) <sup>uCApps</sup> *Linking multiple Cores via MIDI (a special configured MIDI forwarding pipe)*
- [MBNet](#) <sup>uCApps</sup> *The new MIDibox Network utilizing the CAN (Controller Area Network) Interface on the brandnew [PIC18F4685](#) microcontrollers*

From: <https://wiki.midibox.org/> - **MIDibox**

Permanent link: [https://wiki.midibox.org/doku.php?id=core\\_module&rev=1470242110](https://wiki.midibox.org/doku.php?id=core_module&rev=1470242110)

Last update: **2016/08/03 16:35**

