
Envelope Follower

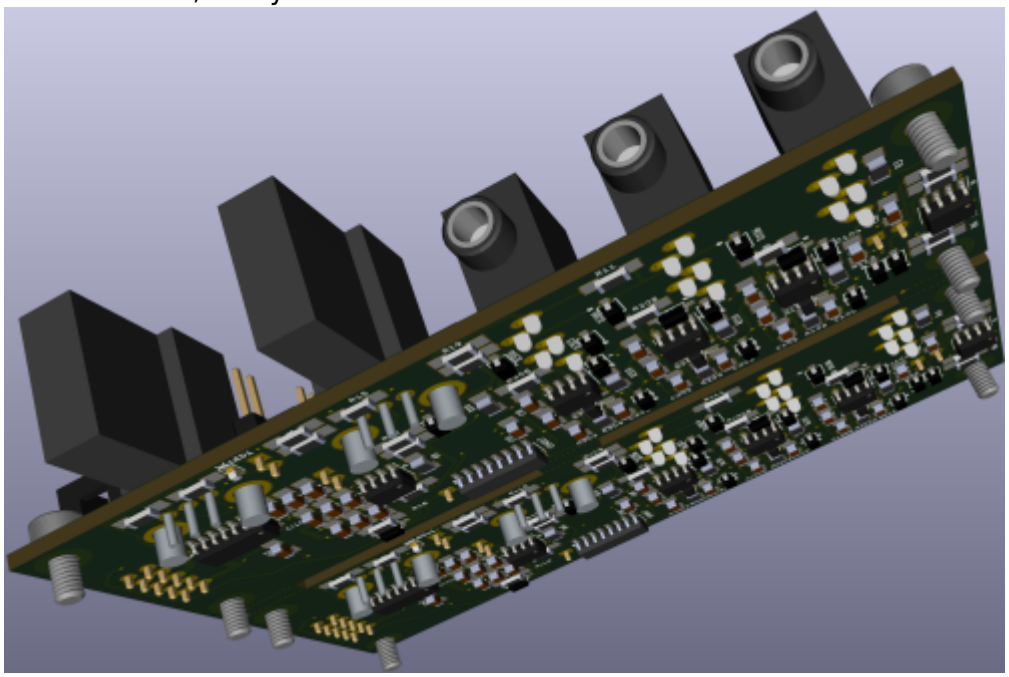based on Harry Bissel
a SMD Variant, ready for Pick and Place



–shown 2 identical boards on one pcb - to save money..

Features

* audio in * Envelope out * Gate out + Gate Threshold-Poti
* Full-wave rectifier
* 3 identical Peakdetectors which are Reseted from a “stepper”
* a Osciallator with tunable Frequency to drive the stepper
* Smoothingcap set via Jumper
* Debugging Jumpers
* PTC and Diode Polarity Protection on the Supply-side


Hardware Requirements

- This Device i build as input module for my CV1 Project, but can be used for other things too
- Soldering Iron - with a Dip that can Handle SMD-Parts, Wires, solder Paste...
- Eurorack Power Source +-12V!

Building

The Design is optimized for Pick and Place most SMD Parts are on the Top-PCB

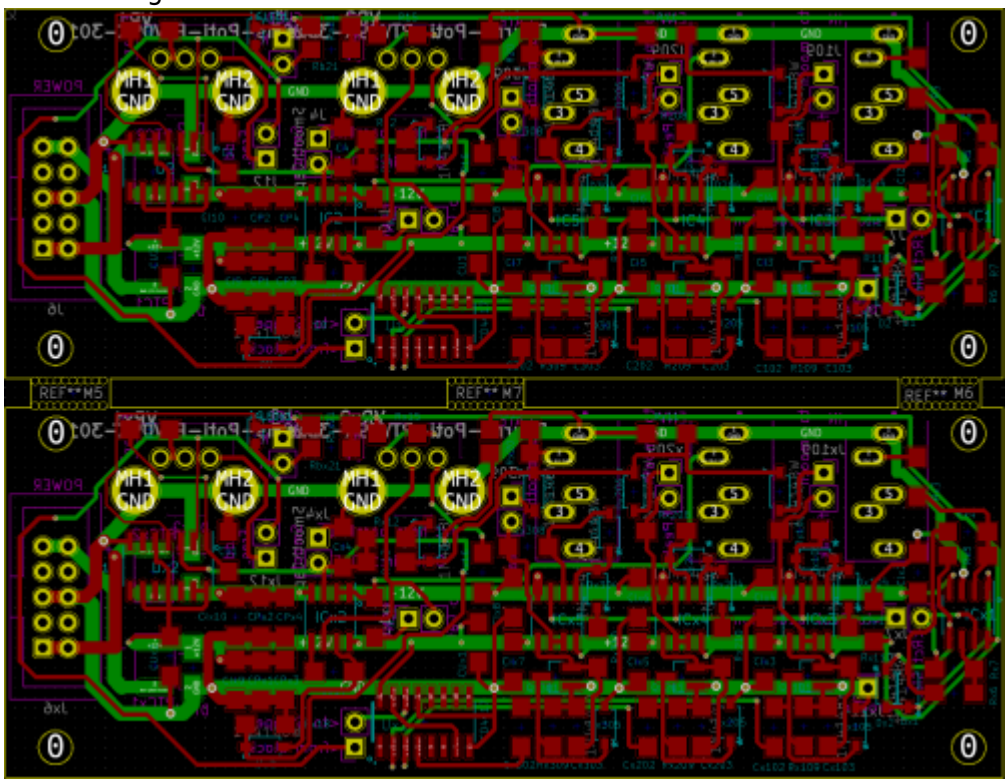i ordered 5 PCBs from JLCPCP with almost all SMD Parts presoldered(except 2 SOIC chips PTC and Protection Diode)
now waiting for Presoldered PCBs



Frontpanel

Fix Me! - Eurorack Alu-Plate

BOM LCSC

these are the parts which are presoldered by the Pick and Place Machine, these are “Basic” Parts
the values with a “x” in it, like Dx1 — are because there are 2 Identical Parts on 1 PCB, because there 2PCBs on 1PCB…. so Dx1 is the same like D1, but its position is on the second board.

Value	Designator	Footprint	LCSC Part Number	Library-Type
100nF	C1,CU1,CI1,CIx1,CUx1,Cx1,CU2,CI2,CIx2,CUx2,CP3,CI3,CIx3,CPx3,CP4,CI4,CIx4,CPx4,C4,Cx4,CI5,CIx5,CI6,CIx6,CI7,CIx7,CI8,CIx8,CI9,CIx9,CI10,CIx10	1206	C24497	
1nF	C102,Cx102,C103,Cx103,C202,Cx202,C203,Cx203,C302,Cx302,C303,Cx303	1206	C35216	
47uF	CP1,CPx1,CP2,CPx2	1206	C96123	
1N4148W	D1,Dx1,D2,Dx2,D7,Dx7,D8,Dx8,D103,Dx103,D104,Dx104,D105,Dx105,D106,Dx106,D203,Dx203,D204,Dx204,D205,Dx205,D206,Dx206,D303,Dx303,D304,Dx304,D305,Dx305,D306,Dx306	SOD123	C81598	
TL072	IC1,ICx1,IC2,ICx2,IC3,ICx3,IC4,ICx4,IC5,ICx5	SOIC-8	C6961	
2N3904	Q101,Qx101,Q201,Qx201,Q301,Qx301	SOT-23	C20526	
100K	R12,Rx12,R13,Rx13,R17,Rx17,R18,Rx18,R108,Rx108,R110,Rx110,R208,Rx208,R210,Rx210,R308,Rx308,R310,Rx310	1206	C17900	
1K	R1,Rx1,R8,Rx8,R11,Rx11,R20,Rx20,Ra21,Rax21	1206	C4410	
2K	R19,Rx19	1206	C17944	
10K	R3,Rx3,R4,Rx4,R5,Rx5,R6,Rx6,R7,Rx7,R15,Rx15,R16,Rx16,R109,Rx109,R209,Rx209,R309,Rx309	1206	C17902	
220	Rb21,Rbx21	1206	C17958	


when making 10Boards…a total of **42,44€** presoledered on the PCBsincl Shipping and Import-Taxes


BOM Mouser

These are the parts which has to be handsoldered
copy list below, and paste in this link, you will need to order the project 2 times since 2PCBs are on 1PCB
583-FM4002|2
490-SJ1-3535NG-GR|3
523-G821EU210AAL10Y|1
650-MINISMDC014F-2|2
771-HEF40106BTD-T|1
595-CD4017BM|1
652-PTV09A-3015FB103|1
652-PTV09A3020FB104|1

for prototyping i ordered:
490-SJ1-3535NG-GR instead of **490-SJ1-3535NG** because it is out of stock - so **GREEN sockets** for now!

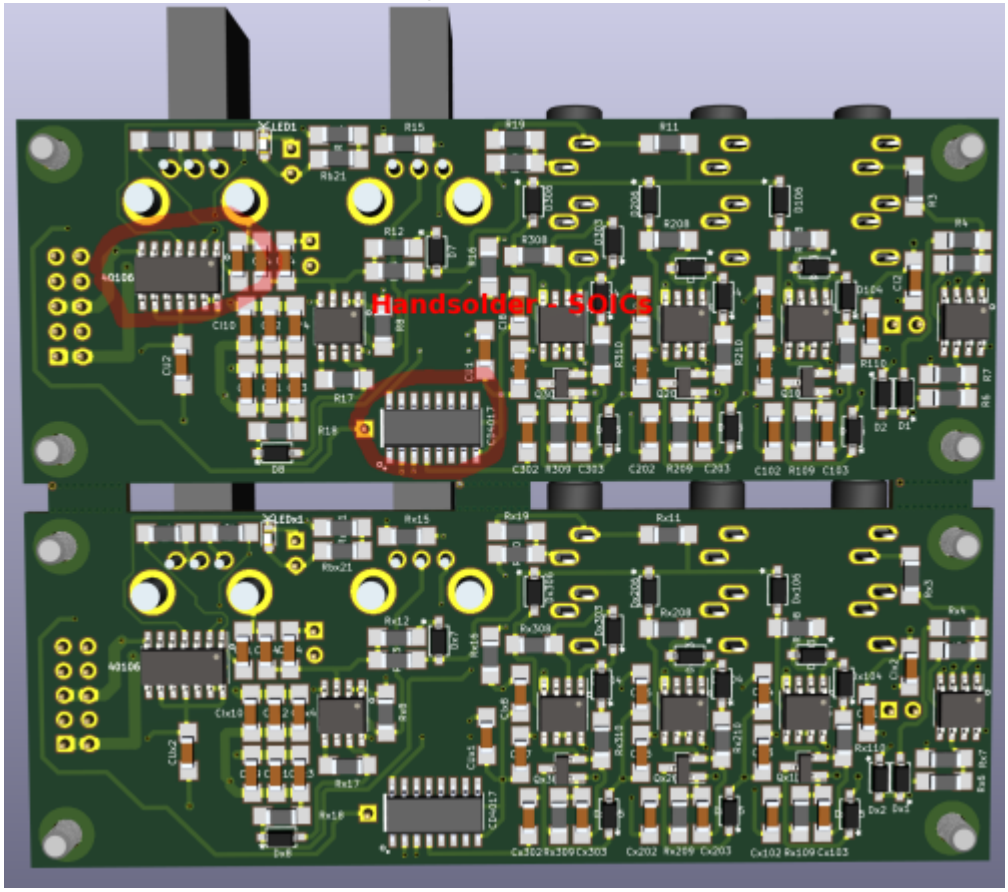when making 10PCBs this make a total of **53,58€** incl Shipping which is free above 50€!
There are 2 SOICs that have to get Handsoldered, i have done this before and its easy!



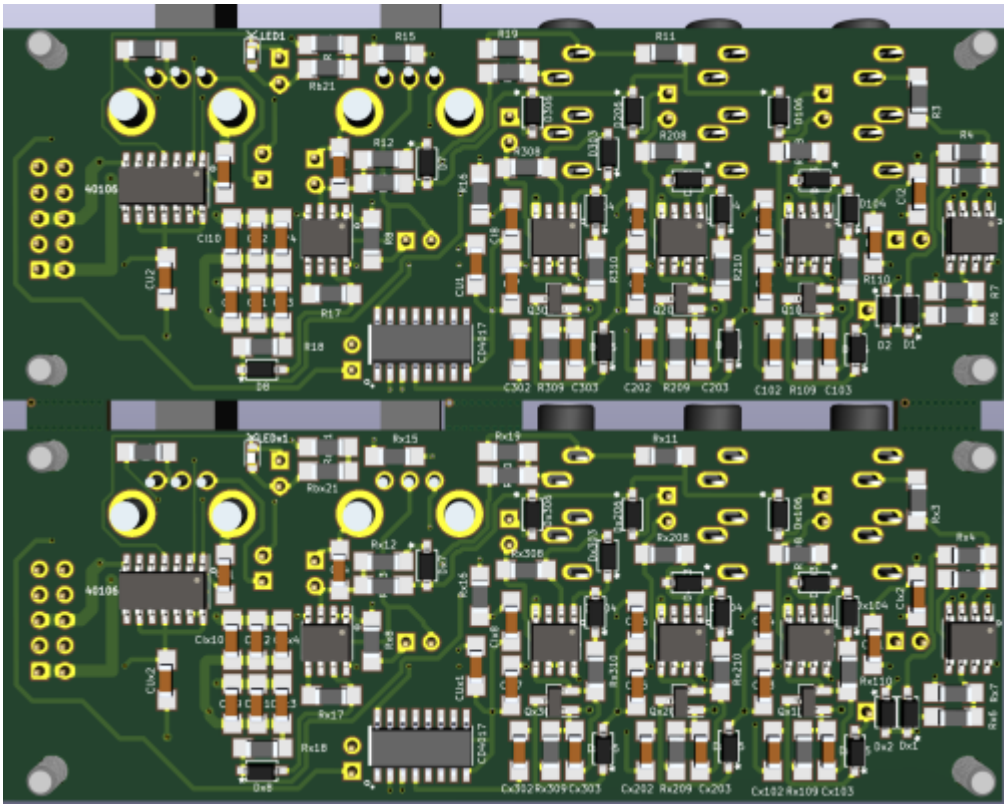the actual Picture is this 

Overall Material Costs

PCB:**42,44€ +** MouserParts:**53,58** = 96,02€ / **10** PCBs **= 9,602€**
(where half off work is done by pick and place machine!)

Kicad Files & Production Files

V1. from 05.01.2021env-follower.zip
Shematic, Board, Gerber, Pick and Place and Booms, ready for Pick and Place!
—at the moment untestet, since i order the project just now!
as Example what you see if you got thru the ordering process:

2021-01-06 | W202101



SMT Assembly

Order #: 23438-2436262A

Build Time: 1 day

5 pcs $28.36

Product Details

bom-LCSC.xls

cpl.xls


Reviewing

File review will be completed in 10-60 mins when business hours.

Merchandise Total: $30.87

Shipping Charge: $18.71

Order Total: $49.58

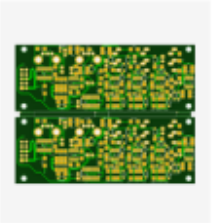

PCB Prototype

Order #: 62A

Build Time: 2-3 days

5 pcs $2.51

Product Details

follow_Y6

Reviewing

File review will be completed in 10-60 mins when business hours.

JLCPCB

JiaLiChuang (HongKong)Co., Limited

Unit 21, 28/F, Metropole Square
No.2 On Yiu Street, Shatin
New Territories
HONG KONG
support@jlcpcb.com
+86 755 23919769
JLCPCB.COM

Invoice No:
Invoice Date: 06/01/2021
Batch No.: W202101

Ship To:

michael sigl
AUSTRIA


Billing To:

michael sigl
AUSTRIA

Description	HS Code	Order Number	QTY	Unit Price	Total
PCB Assembly	73145	1438	5	$5.6720	$28.36
PCB Samples	85340	Y6	5	$0.5020	$2.51

Subtotal:	$30.87
Shipping:	$18.71
Grand Total:	$49.58

Shematic

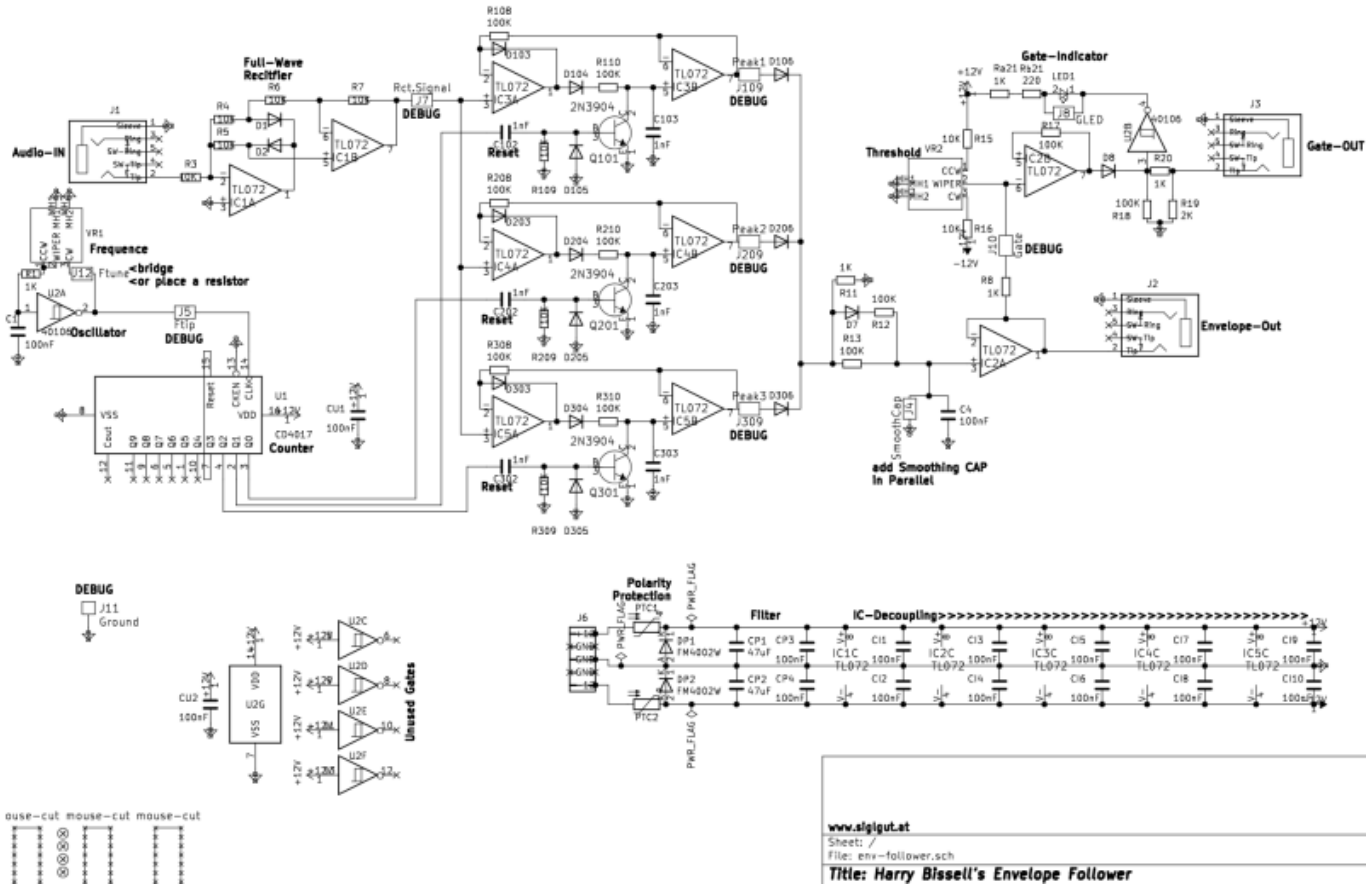

To Do

experiment with the Smooting CAP, i already implimented a Jumper which add a second Capacitor to “double” the capacity… i took 220+220nF, but maybe it is better to use 100+220nF?
experiment with the Frequency Pot which is a lin10K + 2K Serial Resistor which gives a range of 2K-12K - really dont know what value spectrum we need here!
adding some Jumpers to break the circuit for debugging or measurement
frontplate, Debugging First Version

Resources

muffwiggler-topic
modified-shematic
THT-PCB
THT-PCB-Shematic-BUT Attention it is not correct!
THT-PCB-BOM
Haralds-Hi-Clock-Measurements

Community users working on it

- **Phatline** = Programming, Documentation...

Just let a Private message on the forum to user already involved.
I have ProtoBoards here - i test one, and if it works, i can share them for Beta Testing-if you pay the postage

From:
https://wiki.midibox.org/ - **MIDIbox**

Permanent link:
https://wiki.midibox.org/doku.php?id=envelope-follower-bissel-based&rev=1609884879

Last update: **2021/01/05 22:14**