
2025/07/31 10:38 1/5 Envelope Follower
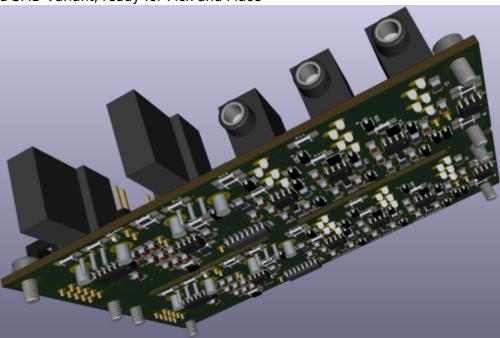
## **Envelope Follower**

based on Harry Bissel a SMD Variant, ready for Pick and Place



-shown 2 identical boards on one pcb - to save money..

### **Features**

- \* audio in \* Envelope out \* Gate out + Gate Threshold-Poti
- \* Full-wave rectifier
- \* 3 identical Peakdetectors which are Reseted from a "stepper"
- \* a Osciallator with tunable Frequency to drive the stepper
- \* Smoothingcap set via Jumper
- \* Debugging Jumpers
- \* PTC and Diode Polarity Protection on the Supply-side

## **Hardware Requirements**


- This Device i build as input module for my CV1 Project, but can be used for other things too
- Soldering Iron with a Dip that can Handle SMD-Parts, Wires, solder Paste...
- Eurorack Power Source +-12V!

## **Building**

The Design is optimized for Pick and Place most SMD Parts are on the Top-PCB

i ordered 5 PCBs from JLCPCP with almost all SMD Parts presoldered(except 2 SOIC chips PTC and Protection Diode)

now waiting for Presoldered PCBs

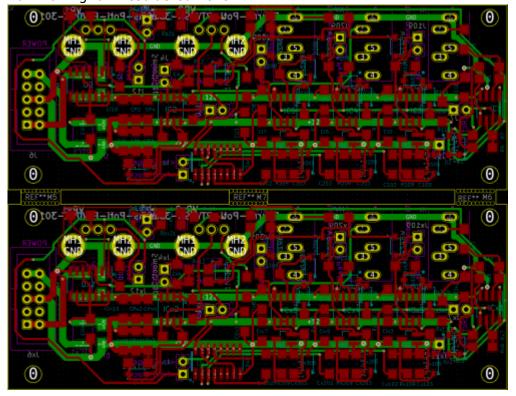

#### **Frontpanel**



### **BOM LCSC**

these are the parts which are presoldered by the Pick and Place Machine, these are "Basic" Parts the values with a "x" in it, like Dx1 — are because there are 2 Identical Parts on 1 PCB, because there 2PCBs on 1PCB.... so Dx1 is the same like D1, but its position is on the second board.

Value	Designator	Footprint	LCSC Part Number	Library-Type
100nF	C1,CU1,Cl1,Clx1,Cux1,Cux1,Cu2,Cl2,Clx2,Cux2,CP3,Cl3,Clx3,CPx3,CP4,Cl4,Clx4,CPx4,C4,Cx4,Cl5,Clx5,Cl6,Clx6,Cl7,Clx7,Cl8,Clx8,Cl9,Clx9,Cl10,Clx10	1206	C24497	
1nF	C102,Cx102,C103,Cx103,C202,Cx202,C203,Cx203,C302,Cx302,C303,Cx203	1206	C35216	
47uF	CP1,CPx1,CP2,CPx2	1206	C96123	
1N4148W	D1,Dx1,D2,Dx2,D7,Dx7,D8,Dx8,D103,Dx103,D104,Dx104,D105,Dx105,D106,Dx106,Dx106,Dx203,Dx203,D204,Dx204,D205,Dx205,D206,Dx206,Dx206,Dx303,Dx303,Dx303,Dx304,Dx304,Dx304,Dx305,Dx306,Dx30	SOD123	C81598	
TL072	C1, Cx1, C2, Cx2, C3, Cx3, C4, Cx4, C5, Cx5	SOIC-8	C6961	
2N3904	Q101,Qx101,Q201,Qx201,Q301,Qx301	SOT-23	C20526	
100K	R12,Rx12,R13,Rx13,R17,Rx17,R18,Rx18,R108,Rx108,Rx108,Rx100,Rx110,Rx208,Rx210,Rx210,Rx308,Rx308,R310,Rx310	1206	C17900	
1K	R1,Rx1,R8,Rx8,R11,Rx11,R20,Rx20,Ra21,Rax21	1206	C4410	
2K	R19,Rx19	1206	C17944	
10K	R3,Rx3,R4,Rx4,R5,Rx5,R6,Rx6,R7,Rx7,R15,Rx15,R16,Rx16,R109,Rx109,R209,Rx209,R309,Rx309	1206	C17902	
220	Rb21,Rbx21	1206	C17958	

when making 10Boards...a total of 42,44€ presoledered on the PCBsincl Shipping and Import-Taxes

http://wiki.midibox.org/ Printed on 2025/07/31 10:38

2025/07/31 10:38 3/5 Envelope Follower

### **BOM Mouser**

These are the parts which has to be handsoldered

copy list below, and paste in this link, you will need to order the project 2 times since 2PCBs are on 1PCB

583-FM4002|2

490-SJ1-3535NG|3

523-G821EU210AAL10Y|1

650-MINISMDC014F-2|2


771-HEF40106BTD-T|1

595-CD4017BM|1

652-PTV09A-3015FB103|1

652-PTV09A3020FB104|1

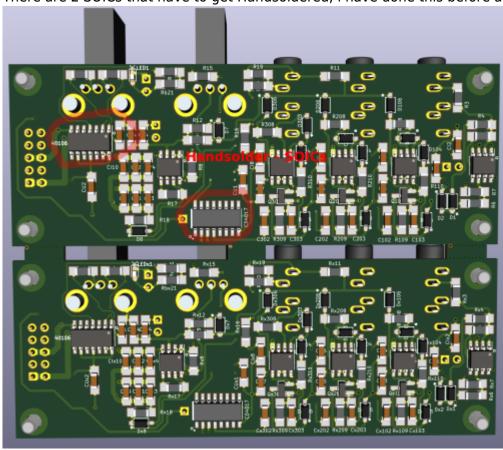when making 10PCBs this make a total of **53,58€** incl Shipping which is free above 50€! There are 2 SOICs that have to get Handsoldered, i have done this before and its easy!



## **Overall Material Costs**

PCB:**42,44€** + MouserParts:**53,58** = 96,02€ / **10** PCBs = **9,602€** (where half off work is done by pick and place machine!)


### **Kicad Files & Production Files**

V1. from 05.01.2021env-follower.zip

Shematic, Board, Gerber, Pick and Place and Booms, ready for Pick and Place!

- —at the moment untestet, since i order the project just now!
- as Example what you see if you got thru the ordering process:

#### **Shematic**

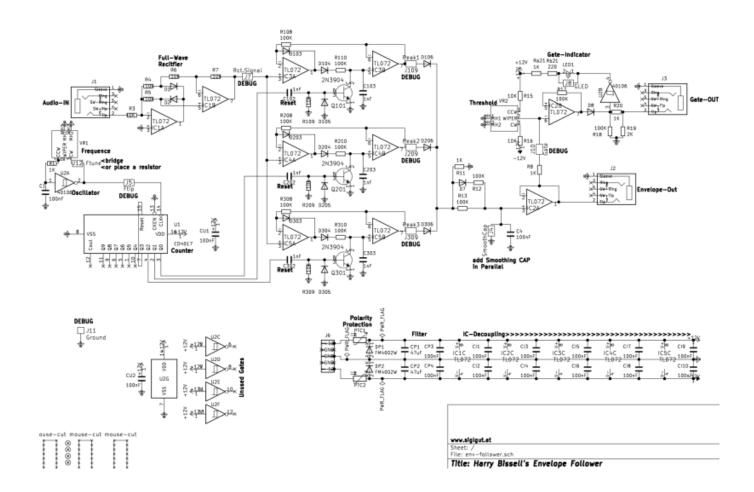

### To Do

experiment with the Smooting CAP, i already implimented a Jumper which add a second Capacitor to "double" the capacity... i took 220+220nF, but maybe it is better to use 100+220nF? experiment with the Frequency Pot which is a lin10K + 2K Serial Resistor which gives a range of 2K-12K - really dont know what value spectrum we need here! adding some Jumpers to break the circuit for debugging or measurement frontplate, Debugging First Version

http://wiki.midibox.org/ Printed on 2025/07/31 10:38

2025/07/31 10:38 5/5 Envelope Follower

### **Resources**

muffwiggler-topic modified-shematic THT-PCB THT-PCB-Shematic-BUT Attention it is not correct! THT-PCB-BOM Haralds-Hi-Clock-Measurements

# Community users working on it

• **Phatline** = Programming, Documentation...

Just let a Private message on the forum to user already involved.

I have ProtoBoards here - i test one, and if it works, i can share them for Beta Testing-if you pay the postage

From:

http://wiki.midibox.org/ - MIDIbox

Permanent link:

http://wiki.midibox.org/doku.php?id=envelope-follower-bissel-based&rev=1609883436

Last update: 2021/01/05 21:50

